

NCERT Class 10 Science - Electricity
Chapter Final Exercise Solutions

Question 1

A piece of wire of resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' , then the ratio R/R' is:

- (a) $1/25$
- (b) $1/5$
- (c) 5
- (d) 25

Answer: (d) 25

Explanation:

1. Resistance of a wire is directly proportional to its length. When the wire is cut into 5 equal parts, the resistance of each part becomes $R/5$.
2. When these 5 parts are connected in parallel, the equivalent resistance R' is calculated as:
$$1/R' = 1/(R/5) + 1/(R/5) + 1/(R/5) + 1/(R/5) + 1/(R/5)$$
$$1/R' = 5/R + 5/R + 5/R + 5/R + 5/R$$
$$1/R' = 25/R$$
3. Rearranging for the ratio:
$$R / R' = 25$$

Question 2

Which of the following terms does not represent electrical power in a circuit?

- (a) $I^2 * R$
- (b) $I * R^2$
- (c) $V * I$
- (d) V^2 / R

Answer: (b) $I * R^2$

Explanation:

1. Electrical power is fundamentally given by $P = V * I$.
 2. According to Ohm's Law, $V = I * R$. Substituting this into the power formula gives $P = (I * R) * I = I^2 * R$.
 3. Alternatively, substituting $I = V / R$ into the power formula gives $P = V * (V / R) = V^2 / R$.
 4. Therefore, $I * R^2$ is not a valid representation of electrical power.
-

Question 3

An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be:

- (a) 100 W
- (b) 75 W
- (c) 50 W
- (d) 25 W

Answer: (d) 25 W

Explanation:

1. Find the resistance (R) of the bulb from its rating using the formula $P = V^2 / R$:
$$R = V^2 / P$$
$$R = (220)^2 / 100$$
$$R = 48400 / 100 = 484 \text{ Ohms}$$
 2. Calculate the power consumed at 110 V using the same resistance:
$$P_{\text{new}} = (V_{\text{new}})^2 / R$$
$$P_{\text{new}} = (110)^2 / 484$$
$$P_{\text{new}} = 12100 / 484 = 25 \text{ W}$$
-

Question 4

Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel

combinations would be:

- (a) 1:2
- (b) 2:1
- (c) 1:4
- (d) 4:1

Answer: (c) 1:4

Explanation:

1. Let the resistance of each wire be R .
 2. In series, total resistance (R_s) = $R + R = 2R$.
 3. Heat produced in series (H_s) = $(V^2 / R_s) * t = (V^2 / 2R) * t$.
 4. In parallel, total resistance (R_p) = $(R * R) / (R + R) = R / 2$.
 5. Heat produced in parallel (H_p) = $(V^2 / R_p) * t = (V^2 / (R/2)) * t = (2 * V^2 / R) * t$.
 6. Ratio of heat produced:
$$H_s / H_p = [(V^2 / 2R) * t] / [(2 * V^2 / R) * t]$$
$$H_s / H_p = (1 / 2) / 2 = 1 / 4$$
Therefore, the ratio is 1:4.
-

Question 5

How is a voltmeter connected in the circuit to measure the potential difference between two points?

Answer:

A voltmeter is always connected in parallel across the two points where the potential difference is to be measured. It is designed with a very high internal resistance so that it draws negligible current from the main circuit, ensuring an accurate voltage reading.

Question 6

A copper wire has diameter 0.5 mm and resistivity of 1.6×10^{-8} Ohm-m. What

will be the length of this wire to make its resistance 10 Ohm? How much does the resistance change if the diameter is doubled?

Answer:

Part 1: Finding the length

- Given:
Diameter (d) = 0.5 mm = 0.5×10^{-3} m
Radius (r) = $d / 2 = 0.25 \times 10^{-3}$ m
Resistivity (ρ) = 1.6×10^{-8} Ohm-m
Resistance (R) = 10 Ohms
- Cross-sectional Area (A) = $\pi \times r^2$
 $A = 3.14 \times (0.25 \times 10^{-3})^2$
 $A = 3.14 \times 0.0625 \times 10^{-6} = 1.9625 \times 10^{-7} \text{ m}^2$
- Formula: $R = \rho \times (l / A)$
 $l = (R \times A) / \rho$
 $l = (10 \times 1.9625 \times 10^{-7}) / (1.6 \times 10^{-8})$
 $l = 1.9625 \times 10^{-6} / 1.6 \times 10^{-8}$
 $l = 122.65 \text{ meters}$

Part 2: If the diameter is doubled

- Resistance is inversely proportional to the square of the diameter (R proportional to $1 / d^2$).
- If the diameter is doubled, the cross-sectional area becomes 4 times larger.
- Consequently, the new resistance will become one-fourth of the original resistance:
New Resistance = $R / 4 = 10 / 4 = 2.5 \text{ Ohms}$.

Question 7

The values of current I flowing in a given resistor for the corresponding values of potential difference V across the resistor are given below –

I (amperes): 0.5, 1.0, 2.0, 3.0, 4.0

V (volts): 1.6, 3.4, 6.7, 10.2, 13.2

Plot a graph between V and I and calculate the resistance of that resistor.

Answer:

Graph Plotting Instructions:

When creating your document, plot 'I' on the X-axis and 'V' on the Y-axis. The data points will form a straight upward-sloping line, demonstrating a linear relationship that verifies Ohm's Law.

Calculation of Resistance:

The resistance (R) corresponds to the slope of the V-I graph.

- Let us pick two points from the data set:

Point 1: $I_1 = 1.0 \text{ A}$, $V_1 = 3.4 \text{ V}$

Point 2: $I_2 = 3.0 \text{ A}$, $V_2 = 10.2 \text{ V}$

- Slope (R) = $(V_2 - V_1) / (I_2 - I_1)$

$$R = (10.2 - 3.4) / (3.0 - 1.0)$$

$$R = 6.8 / 2 = 3.4 \text{ Ohms}$$

The average resistance of the resistor is 3.4 Ohms.

Question 8

When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

Answer:

- Given:

Voltage (V) = 12 V

Current (I) = 2.5 mA = $2.5 \times 10^{-3} \text{ A}$

- Using Ohm's Law ($R = V / I$):

$$R = 12 / (2.5 \times 10^{-3})$$

$$R = (12 \times 1000) / 2.5$$

$$R = 12000 / 2.5 = 4800 \text{ Ohms (or 4.8 kOhms)}$$

The resistance of the unknown resistor is 4800 Ohms.

Question 9

A battery of 9 V is connected in series with resistors of 0.2 Ohm, 0.3 Ohm, 0.4 Ohm, 0.5 Ohm and 12 Ohm, respectively. How much current would flow through the 12 Ohm resistor?

Answer:

- Given resistances in series:
 $R_1 = 0.2 \text{ Ohm}$, $R_2 = 0.3 \text{ Ohm}$, $R_3 = 0.4 \text{ Ohm}$, $R_4 = 0.5 \text{ Ohm}$, $R_5 = 12 \text{ Ohm}$
Voltage (V) = 9 V
 - Total Equivalent Resistance (R_s) = $R_1 + R_2 + R_3 + R_4 + R_5$
 $R_s = 0.2 + 0.3 + 0.4 + 0.5 + 12 = 13.4 \text{ Ohms}$
 - Total current in the circuit (I) = V / R_s
 $I = 9 / 13.4 = 0.67 \text{ A}$
 - In a series circuit, the current remains identical through all components.
 - Therefore, the current flowing through the 12 Ohm resistor is 0.67 A.
-

Question 10

How many 176 Ohm resistors (in parallel) are required to carry 5 A on a 220 V line?

Answer:

- Given:
Resistance of one individual resistor (R) = 176 Ohms
Total Current (I) = 5 A
Total Voltage (V) = 220 V
- Let 'n' be the number of required resistors.
- Total required target resistance (R_p) = V / I
 $R_p = 220 / 5 = 44 \text{ Ohms}$

- For 'n' identical resistors connected in parallel:

$$R_p = R / n$$

$$44 = 176 / n$$

$$n = 176 / 44$$

$$n = 4$$

Exactly 4 resistors connected in parallel are required.

Question 11

Show how you would connect three resistors, each of resistance 6 Ohm, so that the combination has a resistance of (i) 9 Ohm, (ii) 4 Ohm.

Answer:

Case (i) To get 9 Ohms:

- Connect two 6 Ohm resistors in parallel, and then connect this pair in series with the third 6 Ohm resistor.
- Equivalent resistance of the parallel pair (R_p) = $(6 * 6) / (6 + 6) = 36 / 12 = 3$ Ohms.
- Total Resistance (R_{total}) = $R_p + 6 = 3 + 6 = 9$ Ohms.

Case (ii) To get 4 Ohms:

- Connect two 6 Ohm resistors in series, and then connect this entire branch in parallel with the third 6 Ohm resistor.
 - Equivalent resistance of the series branch (R_s) = $6 + 6 = 12$ Ohms.
 - Total Resistance (R_{total}) = $(R_s * 6) / (R_s + 6) = (12 * 6) / (12 + 6) = 72 / 18 = 4$ Ohms.
-

Question 12

Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A?

Answer:

- Given:
Power of one bulb (P) = 10 W
Voltage (V) = 220 V
Maximum allowable current (I) = 5 A
- Resistance of one bulb (R) = V^2 / P
 $R = (220 * 220) / 10 = 48400 / 10 = 4840 \text{ Ohms}$
- Total target resistance allowed for the circuit (R_p) = V / I
 $R_p = 220 / 5 = 44 \text{ Ohms}$
- For 'n' identical bulbs in parallel:
 $R_p = R / n$
 $44 = 4840 / n$
 $n = 4840 / 44$
 $n = 110$

A maximum of 110 lamps can be connected in parallel.

Question 13

A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of 24 Ohm resistance, which may be used separately, in series, or in parallel. What are the currents in the three cases?

Answer:

- Given:
Voltage (V) = 220 V
Resistance of individual coils, $R_a = R_b = 24 \text{ Ohms}$
- Case 1: Coils used separately
Current (I) = $V / R_a = 220 / 24 = 9.17 \text{ A}$
- Case 2: Coils used in series
Total Resistance (R_s) = $24 + 24 = 48 \text{ Ohms}$
Current (I) = $V / R_s = 220 / 48 = 4.58 \text{ A}$

- Case 3: Coils used in parallel
Total Resistance (R_p) = $24 / 2 = 12$ Ohms
Current (I) = $V / R_p = 220 / 12 = 18.33$ A
-

Question 14

Compare the power used in the 2 Ohm resistor in each of the following circuits:

- (i) A 6 V battery in series with 1 Ohm and 2 Ohm resistors, and
- (ii) A 4 V battery in parallel with 12 Ohm and 2 Ohm resistors.

Answer:

- Circuit (i): 6 V battery in series with 1 Ohm and 2 Ohm resistors
Total resistance (R_s) = $1 + 2 = 3$ Ohms
Circuit current (I) = $V / R_s = 6 / 3 = 2$ A
Since it is a series connection, the current through the 2 Ohm resistor is 2 A.
Power used in the 2 Ohm resistor = $I^2 * R = (2)^2 * 2 = 4 * 2 = 8$ W
- Circuit (ii): 4 V battery in parallel with 12 Ohm and 2 Ohm resistors
In a parallel circuit, the voltage across each parallel branch matches the battery voltage.
Voltage across the 2 Ohm resistor = 4 V
Power used in the 2 Ohm resistor = $V^2 / R = (4)^2 / 2 = 16 / 2 = 8$ W

Comparison: The power consumed by the 2 Ohm resistor is exactly the same (8 W) in both electrical configurations.

Question 15

Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V?

Answer:

- Given:
Power of lamp 1 (P_1) = 100 W
Power of lamp 2 (P_2) = 60 W
Voltage (V) = 220 V
- Because the elements are arranged in parallel, total power is the sum of individual powers:
Total Power (P_{total}) = $P_1 + P_2 = 100 + 60 = 160$ W
- Formula for total current: $P_{\text{total}} = V * I$
 $I = P_{\text{total}} / V$
 $I = 160 / 220 = 8 / 11 = 0.73$ A

The total current drawn from the line is 0.73 A.

Question 16

Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?

Answer:

- Energy consumption formula: $E = \text{Power} * \text{Time}$
- For the TV set:
Power = 250 W = 0.25 kW
Time = 1 hour
Energy (E_{tv}) = 0.25 kW * 1 h = 0.25 kWh
- For the Toaster:
Power = 1200 W = 1.2 kW
Time = 10 minutes = 10 / 60 hours = 1 / 6 hours
Energy (E_{toaster}) = 1.2 kW * (1 / 6) h = 0.2 kWh

Conclusion: Comparing 0.25 kWh to 0.2 kWh shows that the TV set uses more energy.

Question 17

An electric heater of resistance 8 Ohm draws 15 A from the service mains 2 hours. Calculate the rate at which heat is developed in the heater.

Answer:

- Given:
Resistance (R) = 8 Ohms
Current (I) = 15 A
Time (t) = 2 hours (Note: The term "rate at which heat is developed" refers directly to Electrical Power, making time an extra piece of information).
- Rate of heat development (Power, P) = $I^2 * R$
 $P = (15)^2 * 8$
 $P = 225 * 8 = 1800 \text{ W (or 1800 Joules per second)}$

The rate at which heat develops is 1800 W.

Question 18

Explain the following:

- (a) Why is the tungsten used almost exclusively for filament of electric lamps?
- (b) Why are the conductors of electric heating devices, such as bread-toasters and electric irons, made of an alloy rather than a pure metal?
- (c) Why is the series arrangement not used for domestic circuits?
- (d) How does the resistance of a wire vary with its area of cross-section?
- (e) Why are copper and aluminium wires usually employed for electricity transmission?

Answer:

- (a) Tungsten has an exceptionally high melting point (approx. 3380 degrees Celsius) and high resistivity. This prevents it from melting or oxidizing easily even when glowing at white-hot temperatures inside a lightbulb.
- (b) Alloys have higher resistivity than their constituent pure metals and possess a significantly higher melting point. They also do not undergo oxidation (burn up) at high operating temperatures.
- (c) In a series circuit, if one appliance fails or is turned off, the entire circuit

breaks, causing all other connected devices to turn off. Additionally, appliances cannot get a uniform voltage line supply in series.

(d) The resistance of a uniform wire is inversely proportional to its cross-sectional area (R proportional to $1/A$). Doubling the thickness decreases the resistance to one-fourth.

(e) Copper and aluminium are excellent electrical conductors with very low values of resistivity. They allow current to pass easily through them while minimizing energy loss as heat during transmission.
